

California State University, Northridge
College of Engineering & Computer Science
Electrical and Computer Engineering
Department

ECE 443L Digital Electronics Laboratory
Report 7


CMOS based Sample and Hold Circuit Design,
Simulation and Experimental Test as well as
Analysis

By Evan Thomas, Haroutun Haroutunian



Abstract:

A sample and hold circuit samples an analog input voltage at a certain point in time and holds the sampled voltage for an extended time after the sample is taken. A sample and hold will keep the sampled analog voltage constant for the length of time necessary to allow an analog to digital converter (ADC) to convert the voltage to a digital form. A basic sample and hold circuit consist of an analog switch, a capacitor, and I/O-Amplifiers.

 


Basic Sample and hold circuit


Sample and hold specifications:


- Aperture time- the time for the analog switch to fully open after the control voltage switches from its sample level to its hold level.
- Aperture jitter- the uncertainty in the aperture time
- Acquisition time - the time required for the device to reach its final value when the control voltage switches from its hold level to its sample level

 - Droop - the change in voltage from the sampled value during the hold interval because of charge leaking off of the hold capacitor
- Feedthrough - the component of the output voltage that follows the input signal after the analog switch is opened. The inherent capacitance from the input to the output of the switches causes feedthrough




Author 1 Case 1, 3, and 5:

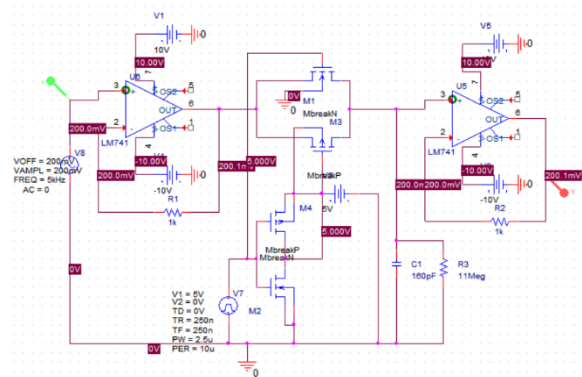

 


Trace Color	Trace Name	Y1	Y2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	0.000			
	X Values	0.000	0.000	0.000					
	V(U6+)	200.016m	200.016m	0.000	15.700u	15.700u	200.016m	200.016m	200.016m
	V(U5.OUT)	200.078m	200.078m	0.000	78.394u	78.394u	200.078m	200.078m	200.078m
	V(U5.OUT)	200.078m	200.078m	0.000	78.394u	78.394u	200.078m	200.078m	200.078m
CURSOR 1,2	V(U6+)	200.000m	200.000m	0.000	0.000	0.000	200.000m	200.000m	200.000m

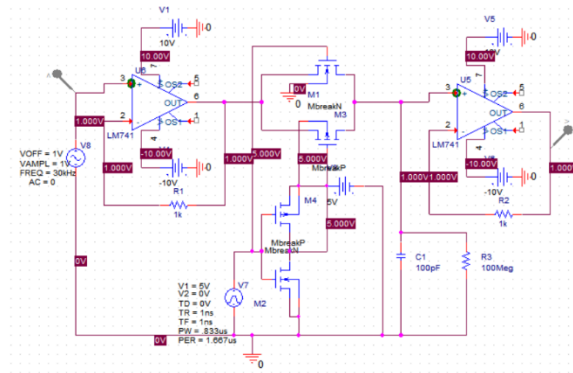Case 1 output when using the components from circuit




 Case 3 circuit with 100pF capacitor and 100 Meg resistor running at a frequency of 30kHz




Trace Color	Trace Name	Y1	Y2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	0.000			
	X Values	0.000	0.000	0.000					
	V(U6+)	1.0000	1.0000	0.000	11.750u	11.750u	1.0000	1.0000	1.0000
	V(U5.OUT)	1.0000	1.0000	0.000	-2.2999p	-2.2999p	1.0000	1.0000	1.0000
CURSOR 1,2	V(U5.OUT)	1.0000	1.0000	0.000	0.000	0.000	1.0000	1.0000	1.0000
	V(U6+)	1.0000	1.0000	0.000	11.750u	11.750u	1.0000	1.0000	1.0000

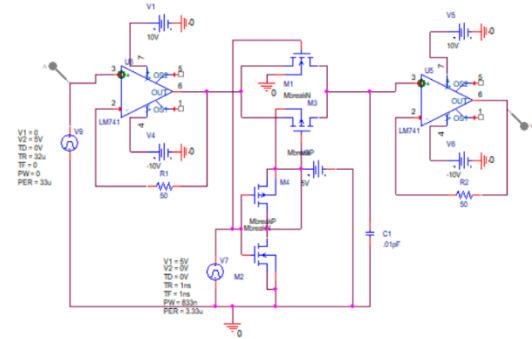Case 3 waveform using the above components.



 Case 5 Ramp circuit with a period of 33 micro seconds or about 30kHz and a .01pF capacitor paired with 50 ohm resistors.






Trace Color	Trace Name	Y1	Y2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	5.0000			
	X Values	32.000u	0.000	32.000u					
CURSOR 1,2	V(V9+)	5.0000	0.000	5.0000	0.000	0.000	5.0000	0.000	2.5000
	V(R2.2)	4.7994	-750.655u	4.8002	-200.570m	-750.655u	4.7994	-750.655u	2.3993

Discharge of the capacitor seems to stay constant and cannot match the ramp circuit perfectly.

Author 2 Case 2, 4, 6:

Experimental Results:

 

  

Author 1 Alternate case 1, 3, and 5:

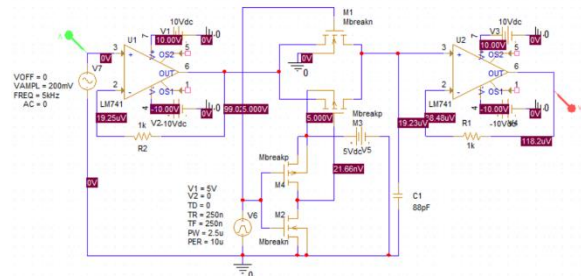


Fig 7.1 Sample and Hold Circuit, $f_{in} = 5\text{kHz}$ and $f_{clk} = 100\text{kHz}$.



Trace Color	Trace Name	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	400.000m		
CURSOR 12	V(U1+)	50.000u	150.000u	-100.000u	0.000	0.000
	V(U1-)	200.000m	-200.000m	400.000m	200.000m	-200.000m
	V(R12)	200.081m	-199.811m	399.891m	80.711u	189.422u

Fig 7.2 Sample and Hold simulation results, $f_{in} = 5\text{kHz}$ and $f_{clk} = 100\text{kHz}$.


 


Fig 7.3 Sample and Hold Circuit, $f_{in} = 40\text{kHz}$ and $f_{clk} = 600\text{kHz}$.

 

Trace Color	Trace Name	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	500.000m		
CURSOR 12	V(V7+)	31.251u	18.750u	12.502u	0.000	0.000
	V(V7-)	250.000m	-250.000m	500.000m	250.000m	-250.000m
	V(R12)	249.974m	-244.596m	494.570m	-26.356u	5.4036m

Fig 7.4 Sample and Hold simulation results, $f_{in} = 40\text{kHz}$ and $f_{clk} = 600\text{kHz}$.

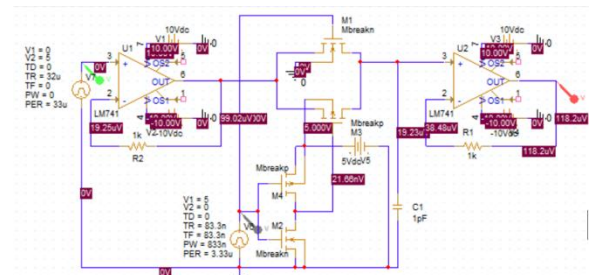


Fig 7.5 Sample and Hold Circuit, $f_{in} = 5\text{kHz}$ Ramp case and $f_{clk} = 33\text{kHz}$.



 


Fig 7.5 Sample and Hold simulation results, $f_{in} = 5\text{kHz}$ Ramp case and $f_{clk} = 33\text{kHz}$.

Conclusion:

In this lab we were able to simulate and experimentally show how a sample and hold circuit works.